



DCS Lab7

Matrix Multiplication

許凱捷


Discrete Cosine Transform

- 本次Lab需要設計計算DCT的電路
- $dct = D A D^T$
- 矩陣D已附在design內(dctmtx)，為fixed-point格式，由1-bit sign, 0-bit integer, 7-bit fraction組成，因此計算過程與整數相同，只需在每完成一次矩陣乘法後將結果除以128即可

```
>> D = dctmtx(4)
```


D =

0.5000	0.5000	0.5000	0.5000
0.6533	0.2706	-0.2706	-0.6533
0.5000	-0.5000	-0.5000	0.5000
0.2706	-0.6533	0.6533	-0.2706

 

Hint

 - 依序將input存入暫存器
- 使用4個乘法器，用內積的方式每cycle進行4個乘法加法算出一個element，將結果除以128後(因為fixed-point乘法) 存入另一組暫存器，共16 cycle
- 經過兩輪矩陣乘法，將結果輸出




DCT.sv



Input Signal	Bit Width	Definition
clk	1	10 ns Clock for 1 cycle
rst_n	1	Asynchronous reset when reset negedge, all output should be zero
in_valid	1	High for 16 cycle
in_data	8	raster scan order 輸入4x4矩陣

Output Signal	Bit Width	Definition
out_valid	1	High for 16 cycle
out_data	10	raster scan order 輸出input矩陣的DCT， 為4x4矩陣

raster scan order

 

Waveform

 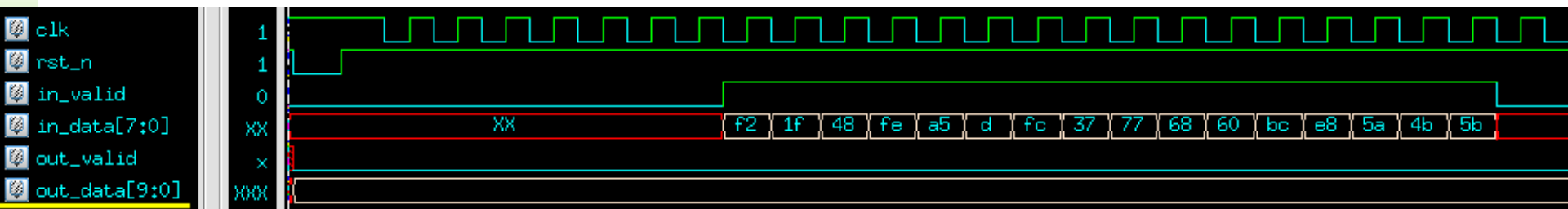

Note

- 請留意乘加法為signed運算
- 注意乘法輸出bit數
- 本次Lab已附上部分FSM和將input存入inbuffer的code，各位同學可基於此繼續完成矩陣乘法部分即可。

```
always_ff@(posedge clk or negedge rst_n)begin
    if(~rst_n)begin
        STATE<=0;
        out_valid<=0;
        out_data<=0;
    end
    else begin
        STATE<=NS;
        out_valid<=
        out_data<=
    end
end

always_comb begin
    case(STATE)
        IDLE:begin
            if(in_valid)    NS = INPUT;
            else            NS = STATE;
        end
        INPUT:begin
            if(~in_valid)   NS =
            else            NS = STATE;
        end
        //next state start matrix multiplication
        //finish your FSM

        OUTPUT:begin
            if(/' ' ')     NS = IDLE;
            else            NS = STATE;
        end
        default:begin
            NS = STATE;
        end
    endcase
end

always_ff@(posedge clk or negedge rst_n)begin
    if(~rst_n)begin
        input_cnt<=0;
    end
    else begin
        if(in_valid)begin
            input_cnt<=input_cnt+1;
        end
        else begin
            input_cnt<=0;
        end
    end
end

always_ff@(posedge clk)begin
    if(in_valid)begin
        inbuffer[input_cnt[3:2]][input_cnt[1:0]]<=in_data;
    end
end
```

Spec

- All outputs must have asynchronous negative-edge reset.
- 01_RTL needs to pass.
- 02_SYN should have no errors or latches.
- 02_SYN's timing slack must be met.
- 03_GATE needs to pass without timing violation.

Command

- `tar -xvf ~dcsta01/Lab07.tar`
- Upload
 - `cd 09_upload`
 - `./01_upload`
 - `./02_download demoX`

Demo1: 4/27(Thursday), 16:20:00

Demo2: 4/27(Thursday), 23:59:59